

## OBJECTIVE | 2 |

### DETERMINATION OF HYDRAULIC COEFFICIENTS FOR CIRCULAR ORIFICE [EXPERIMENTALLY]

#### MATERIALS REQUIRED :

- Supply tank with orifice
- Measuring tank
- Circular orifice plate
- Measuring scale
- Water supply with motor
- Stopwatch
- Needle setup (for jet trajectory tracing)

#### THEORY :

When water flows through an orifice it form a jet whose properties deviate from ideal theoretical behavior due to contraction, friction & turbulence.

The following three coefficients quantify these deviations:

##### Coefficient of Contraction ( $c_c$ ) :

- ratio of area of jet at vena contracta to the area of orifice.

$$\text{i.e., } c_c = \frac{A_{vc}}{A_0}$$

##### Coefficient of velocity ( $c_v$ ) :

- ratio of actual velocity of jet to theoretical velocity

$$\text{i.e., } c_v = \frac{V_{actual}}{V_{th}}$$

##### Coefficient of Discharge ( $c_d$ ) :

ratio of actual discharge to theoretical discharge.

$$c_d = \frac{Q_{act}}{Q_{th}} = c_c \times c_v$$

Also,

$$V_{th} = \sqrt{2gh}$$

$$Q = A \times V = \frac{\text{Volume}}{\text{Time}}$$

$$A_0 = \pi d^2$$

## PROCEDURE:

- 1) ~~FILL~~ <sup>was filled</sup> the supply tank with water using pump until a desired steady head ( $H$ ) is maintained above the orifice centre.
- 2) Measure the head of water above the orifice centre was measured.
- 3) Allow the water flow through orifice & collect the discharged water in measuring tank for known time using a stopwatch.
- 4) The volume of collected water was measured.
- 5) The jet trajectory was traced to measure horizontal distance ( $x$ ) and vertical distance ( $y$ ).
- (6) Finally, the hydraulic coefficients were measured.

## OBSERVATION & CALCULATION:

$$\text{Head of water } (H) = 21.5 \text{ cm}$$

$$x = 22.2 \text{ cm}$$

$$y = 6 \text{ cm}$$

$$\text{Area of orifice } (A_0) = \frac{\pi \times 10^2}{4} = 0.785 \text{ cm}^2$$

$$\Rightarrow V_{th} = \sqrt{2gh}$$

$$= \sqrt{2 \times 981 \times 21.5}$$

$$= 205.38 \text{ cm/s}$$

$$x = vt ; t = \frac{x}{v}$$

$$y = \frac{1}{2} gt^2$$

$$= \frac{1}{2} \times g \times \frac{x^2}{v^2}$$

$$\Rightarrow V^2 = \frac{1}{2} \times 981 \times \frac{(22.2)^2}{6}$$

$$\Rightarrow V = 200.72 \text{ cm/s}$$

$$\therefore \text{Coefficient of velocity } (C_v) = \frac{V}{V_{th}} = \frac{200.72}{205.38} = 0.98$$

For  $C_d$ :

$$\text{Area of measuring tank } (A) = 1200 \text{ cm}^2$$

$$\text{Time } (t) = 30 \text{ s}$$

$$h_1 = 4.1 \text{ cm}$$

$$h_2 = 7.1 \text{ cm}$$

$$h = 3 \text{ cm}$$

$$\therefore \text{Volume of water collected} = 1200 \times 3 = 3600 \text{ cm}^3$$

$$\therefore \text{Actual discharge } (Q_{act}) = \frac{3600}{30} = 120 \text{ cm}^3/\text{s}$$

$$Q_{th} = 0.785 * V_{th} = 0.785 * 205.38 = 161.22 \text{ cm}^3/\text{s}$$

$$\text{Hence, } C_d = \frac{Q_{act}}{Q_{th}} = \frac{120}{161.22} = 0.74$$

$$\text{Finally, } C_c = \frac{C_d}{C_v} = \frac{0.74}{0.98} \frac{0.74}{0.98} = 0.75$$

### RESULT :

→ Coefficient of discharge ( $C_d$ ) = 0.74

→ Coefficient of velocity ( $C_v$ ) = 0.98

→ Coefficient of contraction ( $C_c$ ) = 0.75

### PRECAUTIONS :

→ Maintain constant head during the experiment.

→ Stopwatch reading should be accurate.

→ Take multiple reading to minimize human/instrumental error.

→ Avoid splashes or spillage while collecting water in measuring tank.

## OBJECTIVE | 1 | MEASUREMENT OF VOLTAGE AND CURRENT IN DC CIRCUIT

### EQUIPMENT REQUIRED:

DC Power supply

Multimeter

Bread board

Resistor

Connecting wires

### THEORY :

According to Ohm's law, current ( $I$ ) flowing through a resistor is directly proportional to voltage across it,

$$\text{i.e., } I \propto V$$

$$\Rightarrow I = \frac{1}{R}V ; \frac{1}{R} \text{ is proportionality constant, } R \text{ being resistance}$$

$$\Rightarrow V = IR$$

- In a simple DC circuit consisting of a resistor connected to a voltage source, we can measure:
  - voltage ( $V$ ): across the resistor terminals using a multimeter in voltmeter mode {connected in parallel}
  - current ( $I$ ): through the resistor using a multimeter in ammeter mode {connected in series}.

This experiment demonstrates the fundamental use of a multimeter to measure these parameters in a real DC circuit.

## OBSERVATION :

Table 1:

Voltage (V)	Resistance (R)	Current ( $I = V/R$ )
5V	1 k $\Omega$	4.95 mA
9V	1 k $\Omega$	8.9 mA

## RESULT :

- The voltage & current in a DC circuit were successfully measured using a multimeter
- The experimental values were found consistent with the theoretical calculations.

## PRECAUTIONS:

- 1) Always connect the ammeter in series & voltmeter in parallel
- 2) Double check the polarity before connecting to avoid damaging components.
- 3) Switch off the power supply while making connections.
- 4) Ensure the multimeter is properly set to voltage or current mode before measuring.

## OBJECTIVE | 2 | VERIFICATION OF KRICOFF'S VOLTAGE & CURRENT LAW

### INSTRUMENTS REQUIRED :

DC Power supply

Multimeter

Breadboard

Resistors

Connecting wires

### THEORY :

#### KRICOFF's CURRENT LAW (KCL)

Statement: At any node in an electrical circuit, the sum of currents entering the node is equal to the sum of current leaving the node.  
This is based on conservation of charge.

$$\text{i.e., } \sum I_{\text{in}} = \sum I_{\text{out}}$$

#### Krichooff's Voltage law (KVL)

In any closed loop of an electrical circuit, the algebraic sum of all voltages is zero.

This is based on conservation of energy.

$$\text{i.e., } \sum V_{\text{source}} - \sum V_{\text{drop}} = 0$$

$$\text{or, } \sum V = 0$$

Multimeter is used to measure voltage or current across the loads.

## OBSERVATION :

For KCL:

Voltage = 5V (constant)

Current (I) = 56 mA

Current through  $R_1$  ( $I_1$ ) = 49.9 mA

Current through  $R_2$  ( $I_2$ ) = 4.2 mA

Current through  $R_3$  ( $I_3$ ) = 2.1 mA

Verification:

$$\begin{aligned} I_1 + I_2 + I_3 &= 49.9 + 4.2 + 2.1 \\ &= 56.2 \approx 56 \\ &= I \quad \text{H} \end{aligned}$$

For KVL:

Source voltage = 9V

Voltage drop through ( $R_1$ ) = 3.1V

Voltage drop through ( $R_2$ ) = 2.2V

Voltage drop through ( $R_3$ ) = 3.9V

Verification:

$$\sum V_{\text{source}} - \sum V_{\text{drop}} = 0$$

$$\Rightarrow 9 - [3.1 + 2.2 + 3.9] = 0$$

$$\Rightarrow 0.2 \approx 0 \quad \text{H}$$

## RESULTS :

→ Kirchhoff's Current law (KCL) was verified at the node.

→ Kirchhoff's Voltage law (KVL) was verified in the loop.

## PRECAUTIONS :

(i) Ensure all connections are tight and correct before powering the circuit.

(ii) Connect ammeter in series & voltmeter in parallel.

(iii) Switch off the power supply before modifying the circuit.

### OBJECTIVE | 3 | :

### VERIFICATION OF OHM'S LAW

### EQUIPMENTS REQUIRED:

DC Power supply

Multimeter

Resistor

Breadboard

Connecting wires

### THEORY:

Ohm's law states that the current ( $I$ ) flowing through a conductor is directly proportional to the voltage ( $V$ ) across two points, provided the temperature & other physical conditions remain same.

$$\text{i.e., } I \propto V$$

$$\Rightarrow I = \frac{1}{R} V$$

$$\Rightarrow V = IR \quad ; \quad R = \text{resistance of conductor.}$$

A graph plotted between voltage & current should be a straight line or linear, confirming the Ohm's law.

### OBSERVATION TABLE:

V	I	$R = V/I$
0.17	0.15	1.133
0.35	0.30	1.167
0.66	0.57	1.157
1.12	0.96	1.167
1.73	1.47	1.176
2.27	1.93	1.176
3.07	2.60	1.180
3.56	3.01	1.182
4.50	3.83	1.174
5.09	4.33	1.175

## RESULT :

The experiment confirms that the current increases linearly with voltage, keeping resistance constant (approximately).

Hence, Ohm's law is verified.

## PRECAUTIONS :

- (i) Connect the multimeter correctly for current & voltage measurements
- (ii) Take multiple readings for more accurate results.
- (iii) ~~Ensure~~ Ensure all connections are tight and secure before switching on the power.
- (iv) Keep the temperature & other physical conditions constant.

# plot graph yourself guys!!

07/08/2025

## OBJECTIVE - 4

MEASUREMENT OF AMPLITUDE, FREQUENCY, TIME PERIOD, Average and RMS VALUE USING OSCILLOSCOPE

## EQUIPMENTS USED:

Oscilloscope

Function generator

Connecting probes

Power supply (AC)

## THEORY:

A cathode ray oscilloscope is a powerful electronic test instrument used to observe varying signal voltages. It displays the waveform of electrical signals and enables measurement of various parameters.

Amplitude (A) : Maximum vertical deflection of waveform (volts)

Time period (T) : Time taken to complete one full cycle of waveform.

Frequency (f) : The number of cycles per second.

$$f = \frac{1}{T}$$

Average value ( $V_{avg}$ ) = For a full sine wave, average value over a period is zero.

So, over a half cycle

$$V_{avg} = \frac{2}{\pi} A$$

RMS value ( $V_{rms}$ ) = Root mean square value of sinusoidal waveform

$$\therefore V_{rms} = \frac{A}{\sqrt{2}}$$

These values can be measured directly from the waveform displayed on CRO screen by counting divisions & multiplying by the scale (volts / div or time / div)

## OBSERVATION & CALCULATION

$$\text{Amplitude} = 2 \text{ divisions} \times 1 \text{ V/div}$$
$$= 2 \text{ Volts}$$

$$\text{Time period}(T) = 3.4 \text{ divisions} \times 0.1 \text{ ms/div}$$
$$= \cancel{2.942} \times 10$$
$$= 0.34 \times 10^{-3} \text{ s}$$

$$\text{Frequency } (f) = \frac{1}{T} = \frac{1}{0.34 \times 10^{-3}} = 2.942 \text{ kHz}$$

$$V_{\text{Average}} = \frac{2}{\pi} \times 2 = 1.27 \text{ V}$$

$$V_{\text{rms}} = \frac{2}{\sqrt{2}} = \cancel{1.41} \text{ V}$$

Frequency of wave generated in function generator = 2.56 kHz

Difference in frequency of wave observed in CRO & wave generated in function generator =  $2.942 - 2.56$

$$= 0.382 \text{ kHz}$$

This shows that CRO is very sensitive instrument.

### RESULT:

→ The amplitude, time period, frequency, Average & RMS values of the input sine wave were measured using oscilloscope.

### PRECAUTION:

- (i) Set appropriate volt/div and time/div settings to avoid distorted waveforms.
- (ii) Always calibrate the oscilloscope before taking readings.
- (iii) Take readings only after waveform is stable.
- (iv) Handle probe connections carefully to prevent loose contact.

## OBJECTIVE | 5

TO STUDY V-I CHARACTERISTICS OF A PN-JUNCTION DIODE IN FORWARD BIAS CONDITION

## APPARATUS REQUIRED:

PN JUNCTION Diode characteristic Apparatus

Variable DC Power Supply

Connecting probes

## THEORY | 1:

A PN-junction diode allows current to pass in only one direction which is called forward biasing of the diode.

In reverse bias, it offers high resistance & negligible current.

In forward bias condition, P-side of diode is connected to positive terminal & current increases exponentially after threshold voltage ( $\sim 0.3\text{V}$  for Ge).

The V-I graph is non-linear.

## OBSERVATION Table:

Volt division	V (volt)	I (mA)
0	0	0
1	0.05	0
2	0.1	0
3	0.15	0
5	0.25	0.2
6	0.30	0.4
7	0.35	1
10	0.5	1
12	0.6	1.4
15	0.75	1.8
20	1	2.8
25	1.25	3.8
30	1.5	4.8
40	2	6.8
50	2.5	8.8
57	2.85	10
60	3	~

3V -dc

60 divisions  $\rightarrow 3\text{V}$

1 div  $\rightarrow \frac{1}{60}\text{V}$

mA - current

50 divisions  $\rightarrow 10\text{mA}$

1 div  $\rightarrow \frac{1}{50}\text{mA}$

## RESULT :

→ The forward bias characteristics of PN junction diode shows a non linear rise in current after the threshold voltage ( $\sim 0.3V$ ).

## PRACTICAL PRECAUTIONS

- Ensure all connections are tight & correct.
- Ensure there is correct polarity in the circuit components.
- Avoid Parallax error while observing the value.